

为什么先求电压？
 ← 因为电容隔直通交，流过电流一样，电容不知

$$\begin{cases}
 \begin{array}{c}
 + \\
 -
 \end{array} \frac{1}{C_1} \\
 \begin{array}{c}
 + \\
 -
 \end{array} \frac{1}{C_2}
 \end{cases}
 \begin{array}{l}
 i = \frac{dq}{dt} \quad i = C \frac{du}{dt} \\
 V_1 = \frac{1}{C_1} \int_{-\infty}^t i(s) ds \\
 V_2 = \frac{1}{C_2} \int_{-\infty}^t i(s) ds
 \end{array}$$

$$U = V_1 + V_2 = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int_{-\infty}^t i(s) ds = \frac{1}{C} \int_{-\infty}^t i(s) ds$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

$$V = \frac{1}{C} \int_{-\infty}^t i(s) ds$$

$$V = V_1 + V_2$$

$$V_1 C_1 = V_2 C_2 = VC$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$V_1 = \frac{C}{C_1} V = \frac{C_2}{C_1} V_2$$

$$V_2 = \frac{C}{C_2} V = \frac{C_1}{C_2} V_1$$

$$V_1 = \frac{C}{C_1} V = \frac{C_1 C_2}{C_1 + C_2} \cdot \frac{1}{C_1} V = \frac{C_2}{C_1 + C_2} V$$

$$V_2 = \frac{C}{C_2} V = \frac{C_1 C_2}{C_1 + C_2} \cdot \frac{1}{C_2} V = \frac{C_1}{C_1 + C_2} V$$

串联分压 类似电流分流