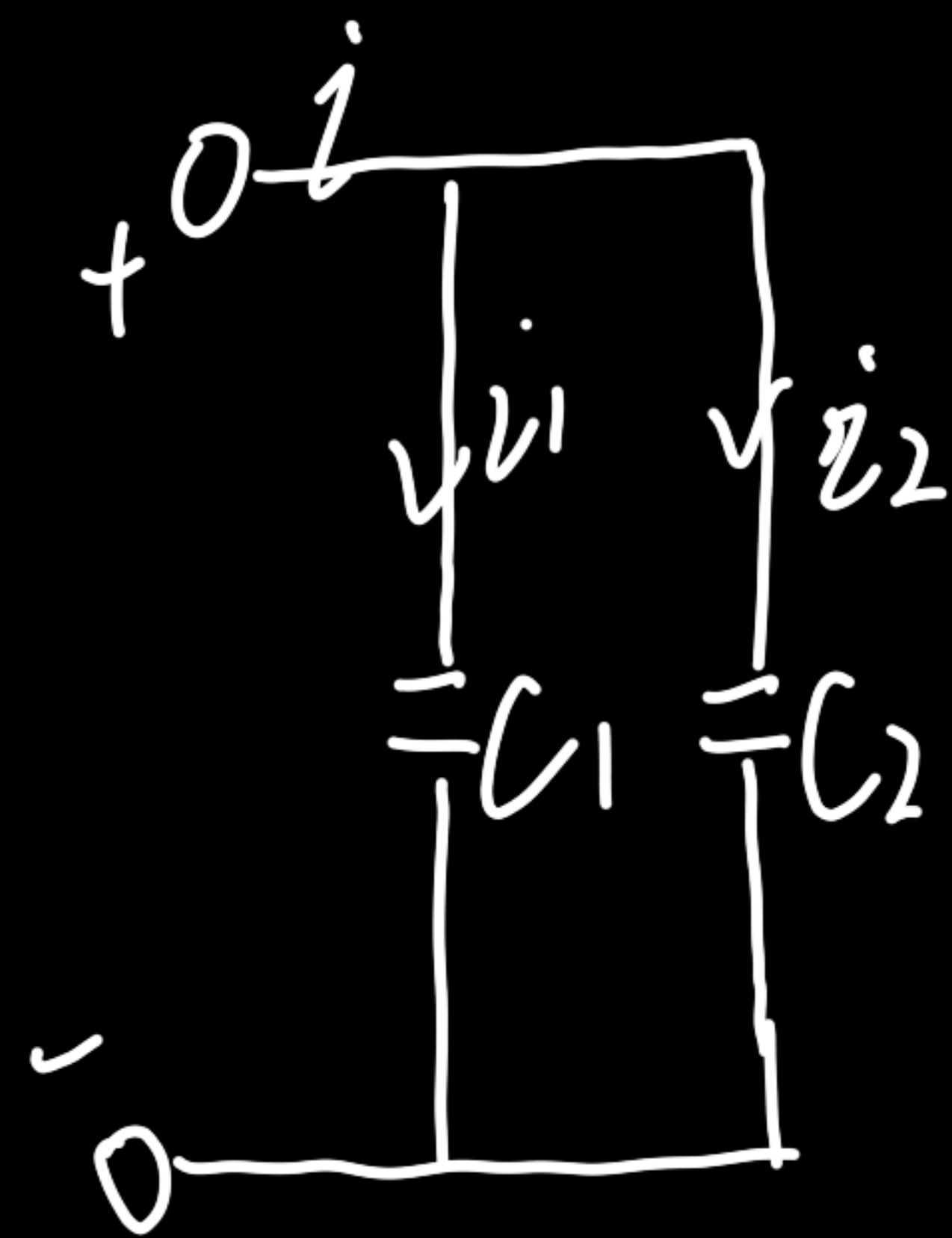




$$i_1 = C_1 \frac{dv}{dt} \quad i_2 = C_2 \frac{dv}{dt}$$

$$i = i_1 + i_2 = (C_1 + C_2) \frac{dv}{dt} = C \frac{dv}{dt}$$

$$i_1 = \frac{C_1}{C} i$$

$$i_2 = \frac{C_2}{C} i$$

容

导

串

$$C = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

并

$$C = C_1 + C_2$$

$$C_1 = C + C_2$$

电容和电导
→ 同构