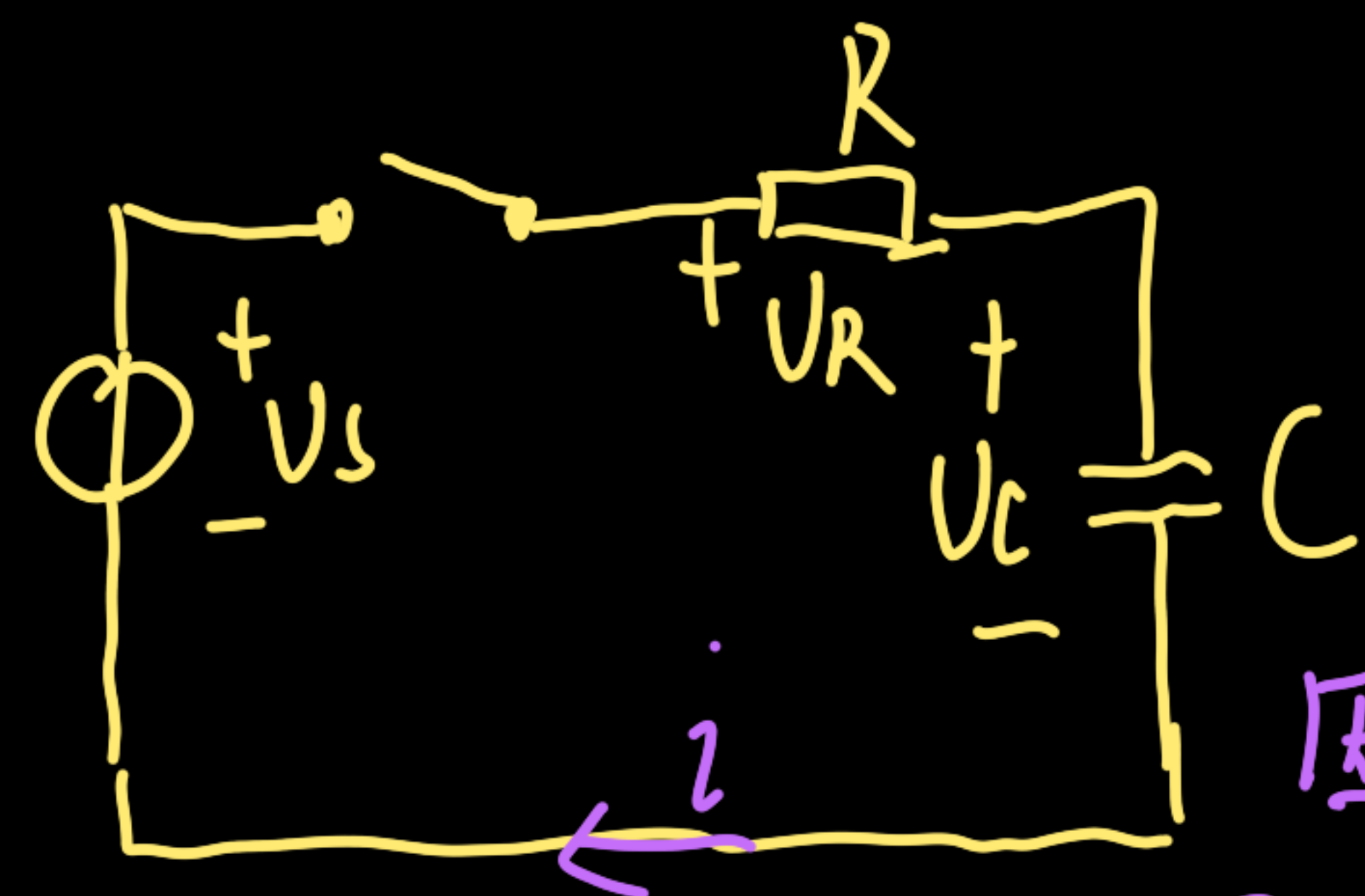




$$RC \frac{dU_C}{dt} + U_C = U_s \quad U_C = U_C' + U_C''$$

因为 \$U_s\$ 为常数, 设非齐次特解 \$U_C'' = C_0\$

则 \$0+ C_0 = U_s \quad U_C'' = U_s\$



$$U_C' = A e^{-\frac{t}{RC}} \quad U_C(0-) = U_C(0+) = A e^{-\frac{0}{RC}} + U_s = 0 \quad A = -U_s$$

$$\text{则 } U_C = -U_s e^{-\frac{t}{RC}} + U_s = U_s (1 - e^{-\frac{t}{RC}})$$

$$i = C \frac{dU_C}{dt} = \frac{U_s}{R} e^{-\frac{t}{RC}}$$

电源对电路的控制

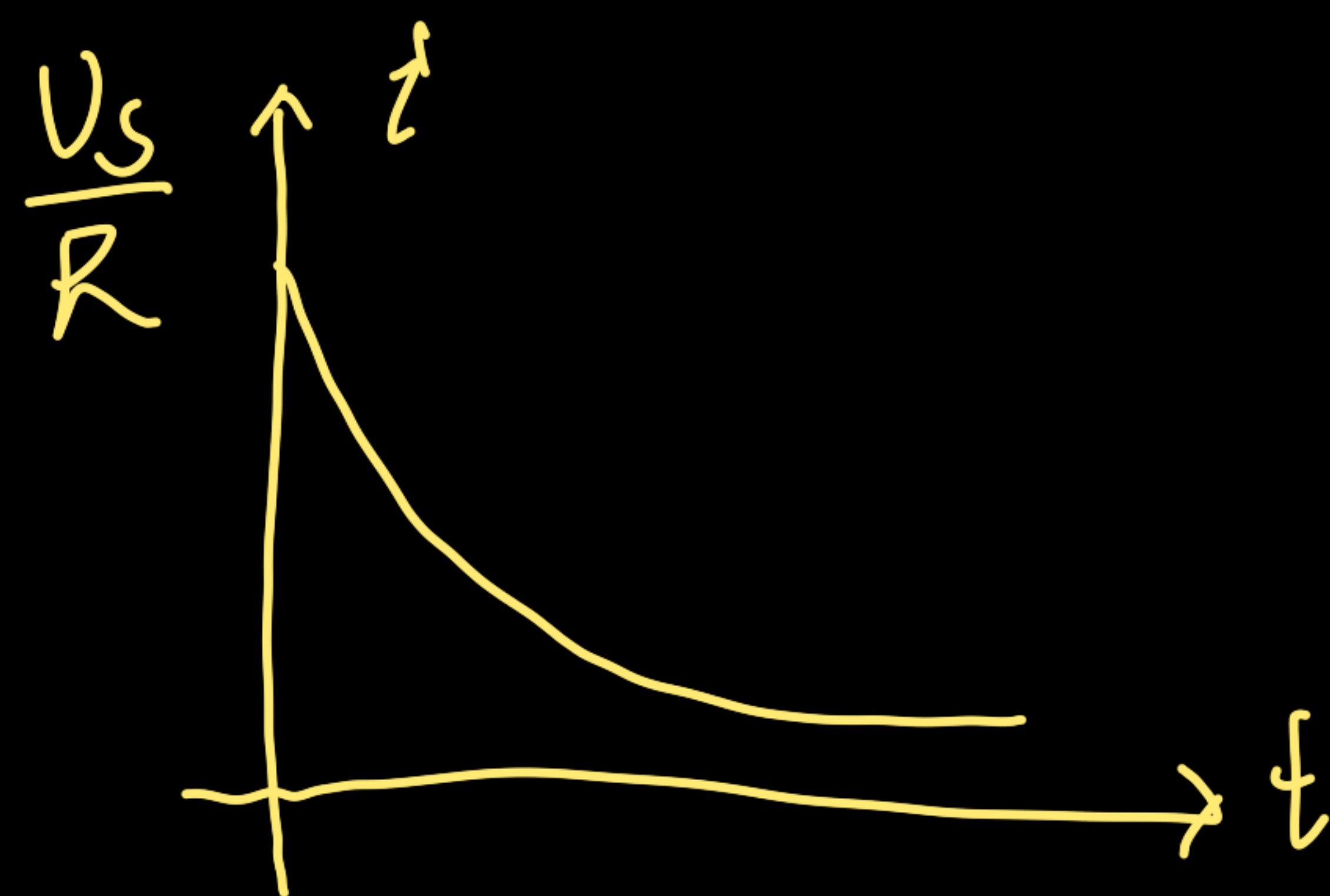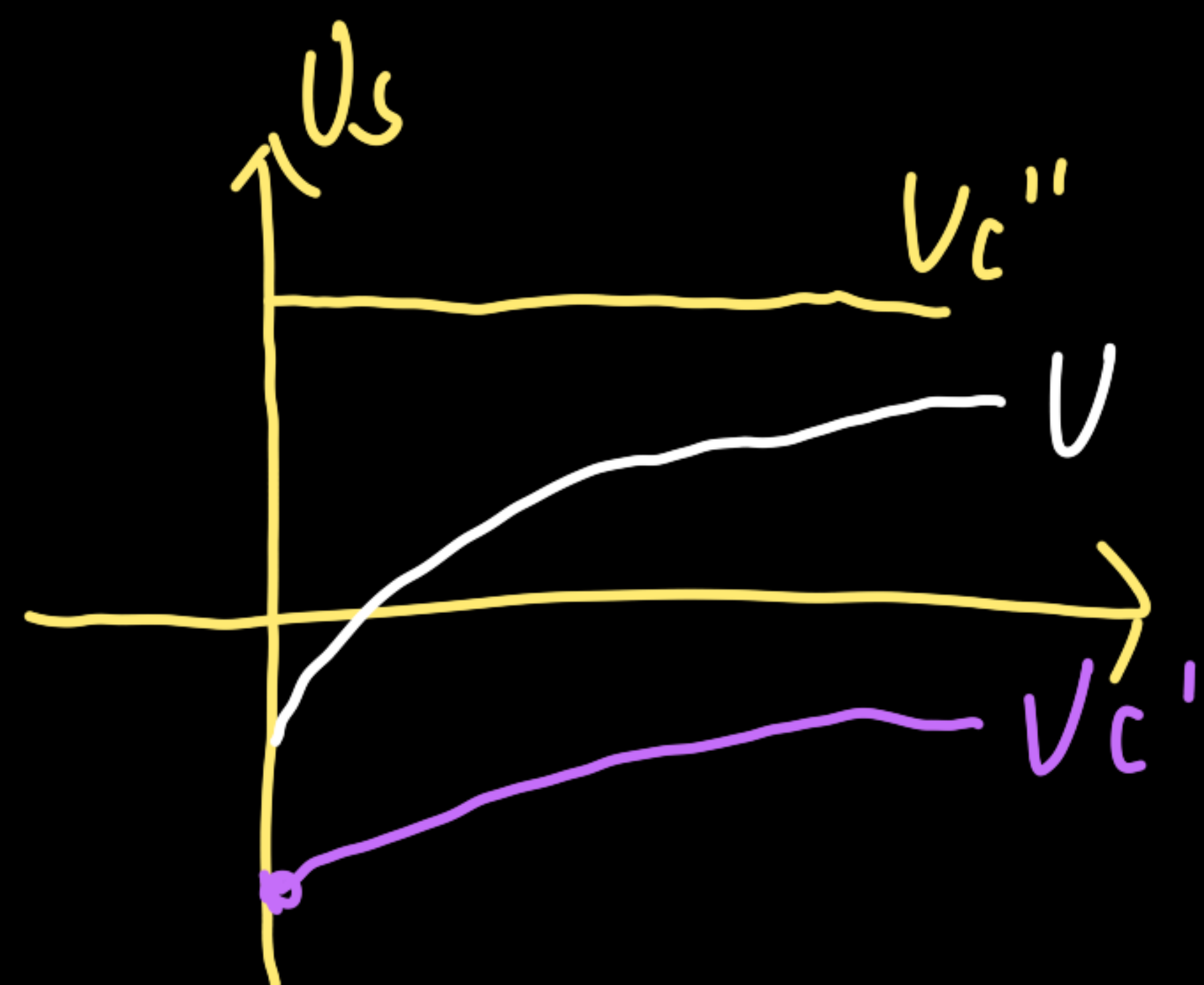非齐次特解 \$\rightarrow U_s \rightarrow\$ 强制分量, 稳态分量
齐次通解 \$\rightarrow RC \frac{dU_C}{dt} + U_C \rightarrow\$ 自由分量, 暂态分量



↓
电路除电源内部的互相影响