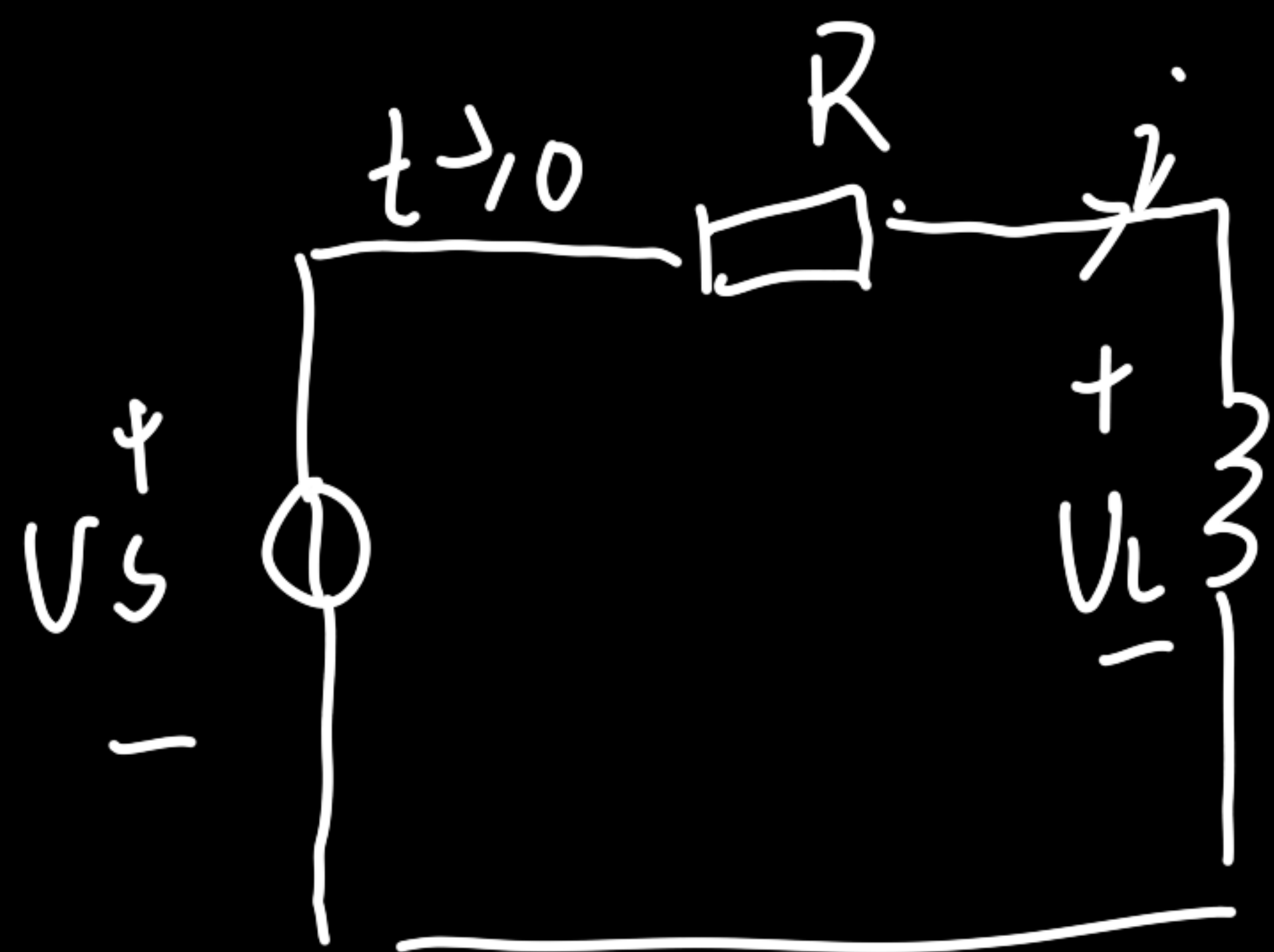




未动作

$$V_L = 0$$

断开


$$i \neq 0$$

$$i = \frac{V_s}{R}$$

$$V_L = L \left(\frac{di}{dt} \right) \rightarrow \infty$$

切断电感出现过电压

$$V_L \rightarrow \infty$$

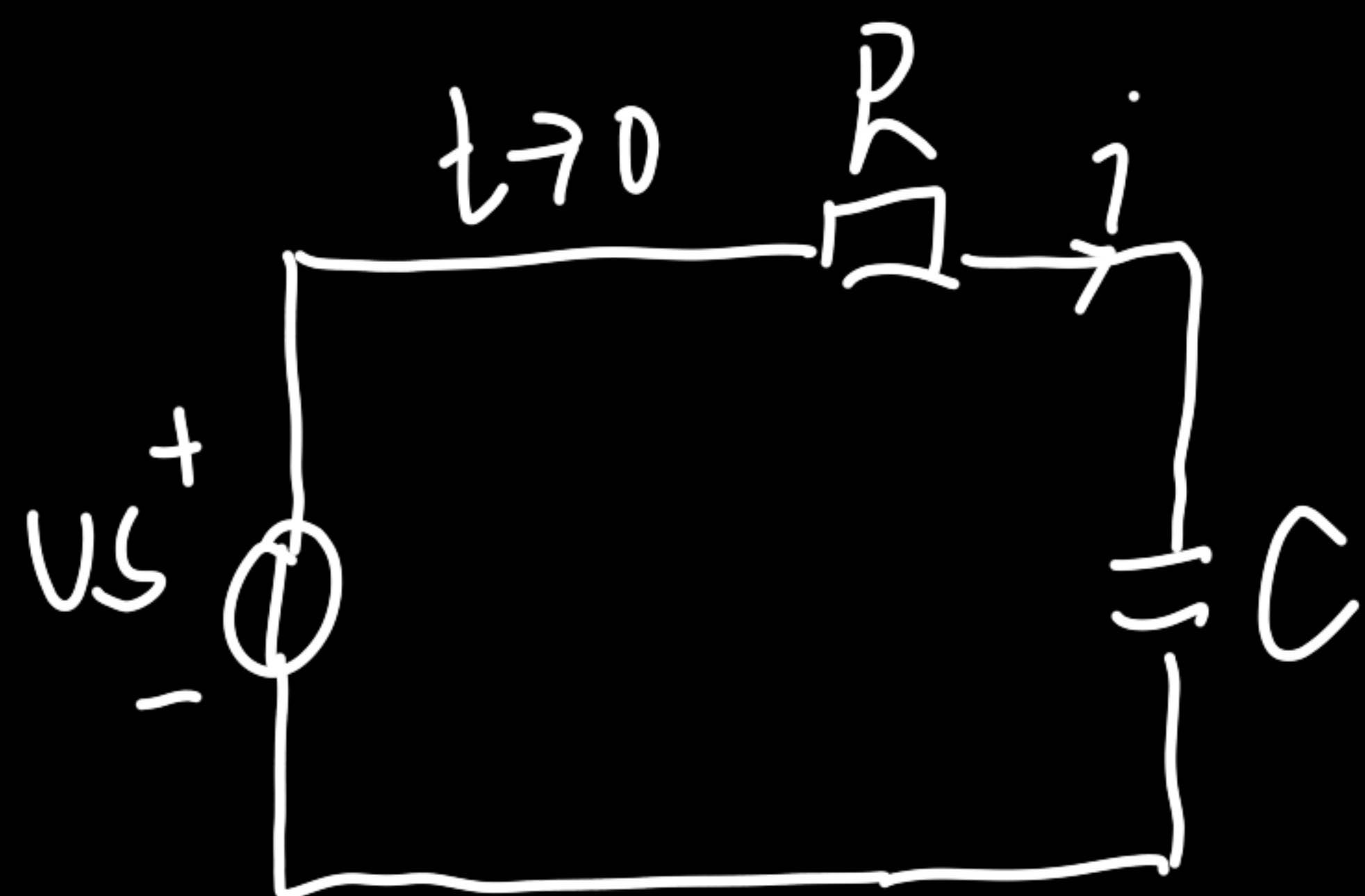


未断开

0^-

$$V_C = V_s$$

0^+

$$V_C^+ = 0$$

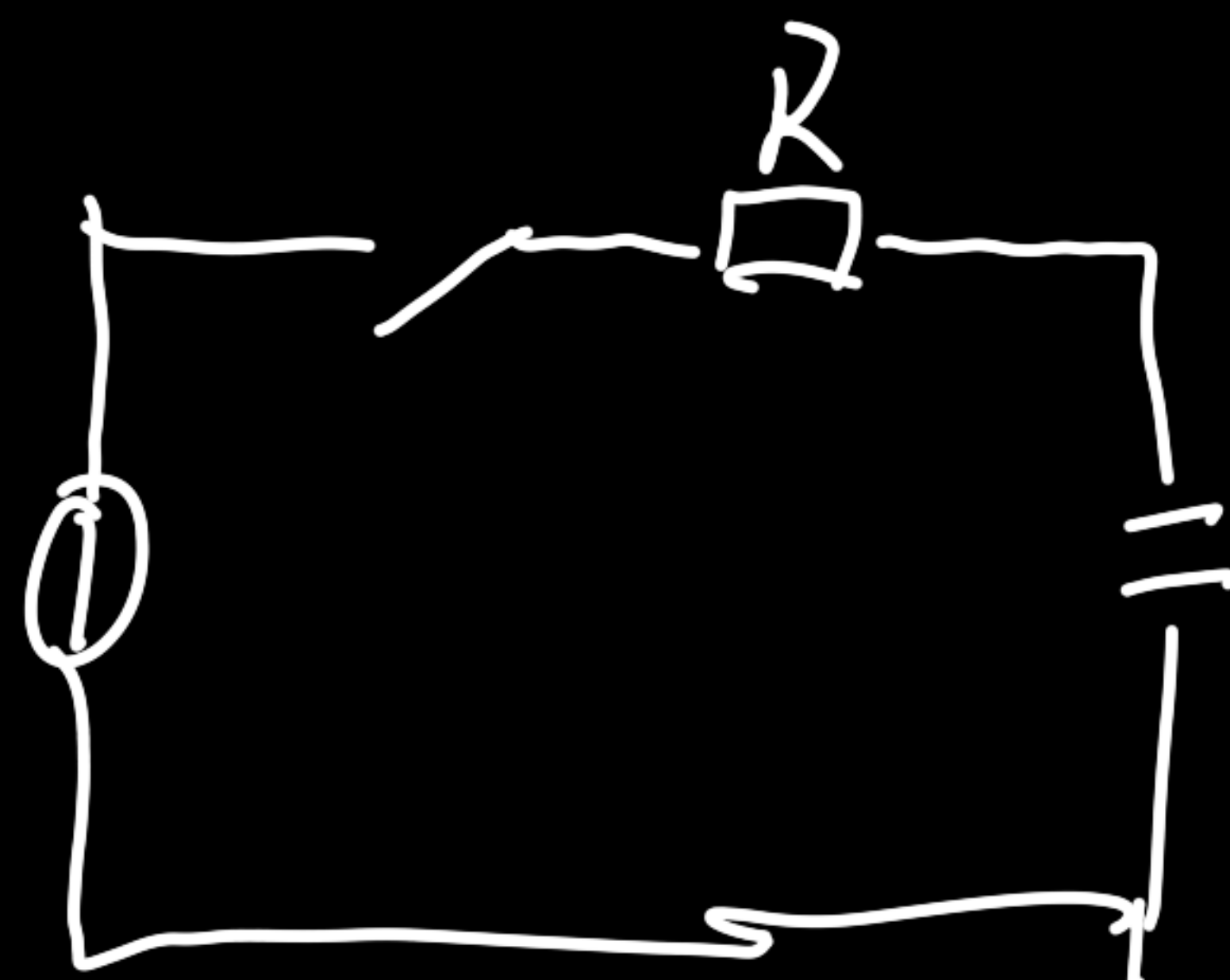

$$i_C = \frac{dV_C}{dt} \rightarrow \infty$$

切断电容出现过电流

$$i_C \rightarrow \infty$$