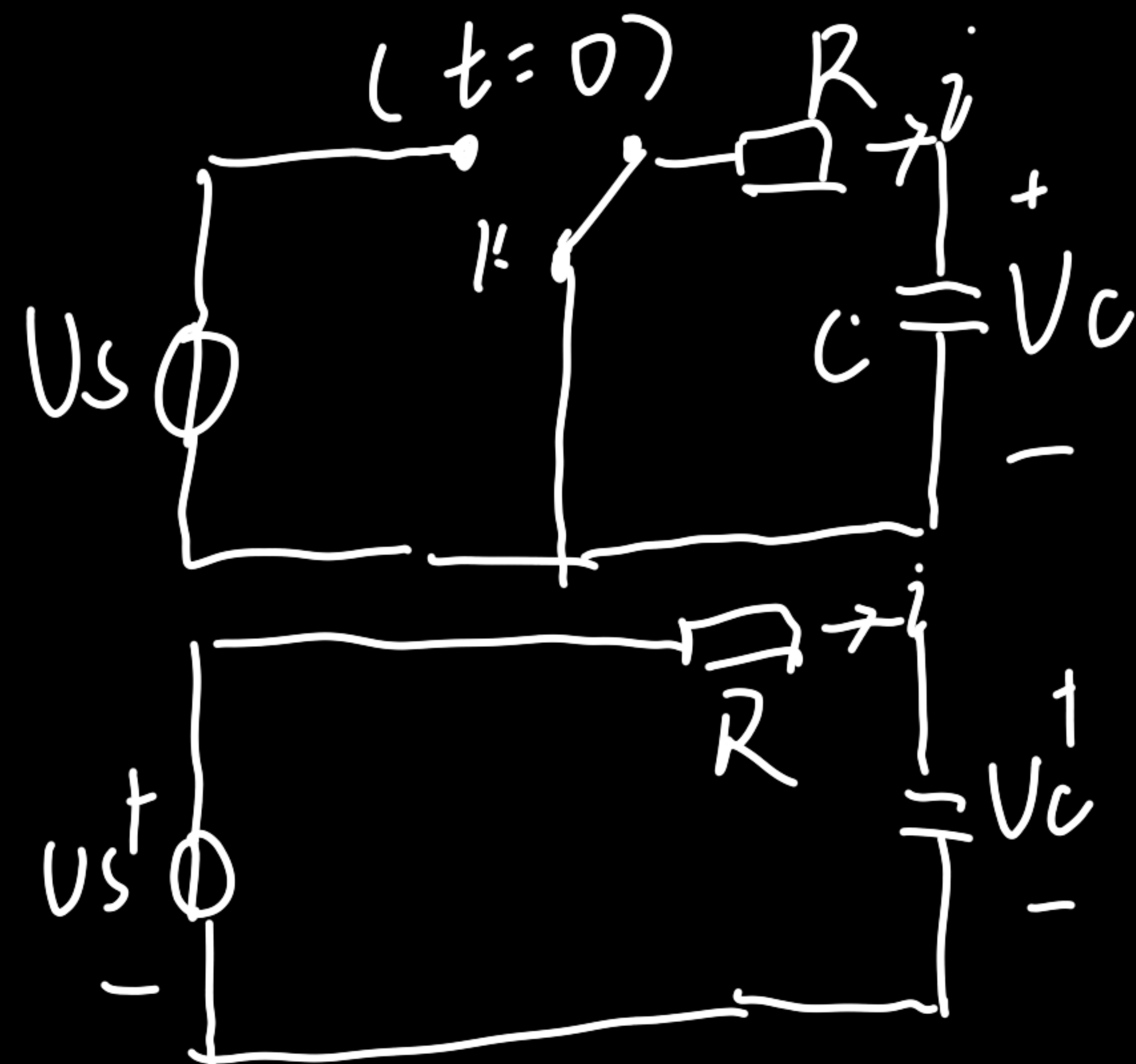


电容电路




电路定理成立, 逐渐变化

$$t = 0^- \quad i = 0 \quad V_C = 0$$


$$t = 0^+ \quad i = \frac{U_s}{R}$$

V_C 无突变 i_C 突变

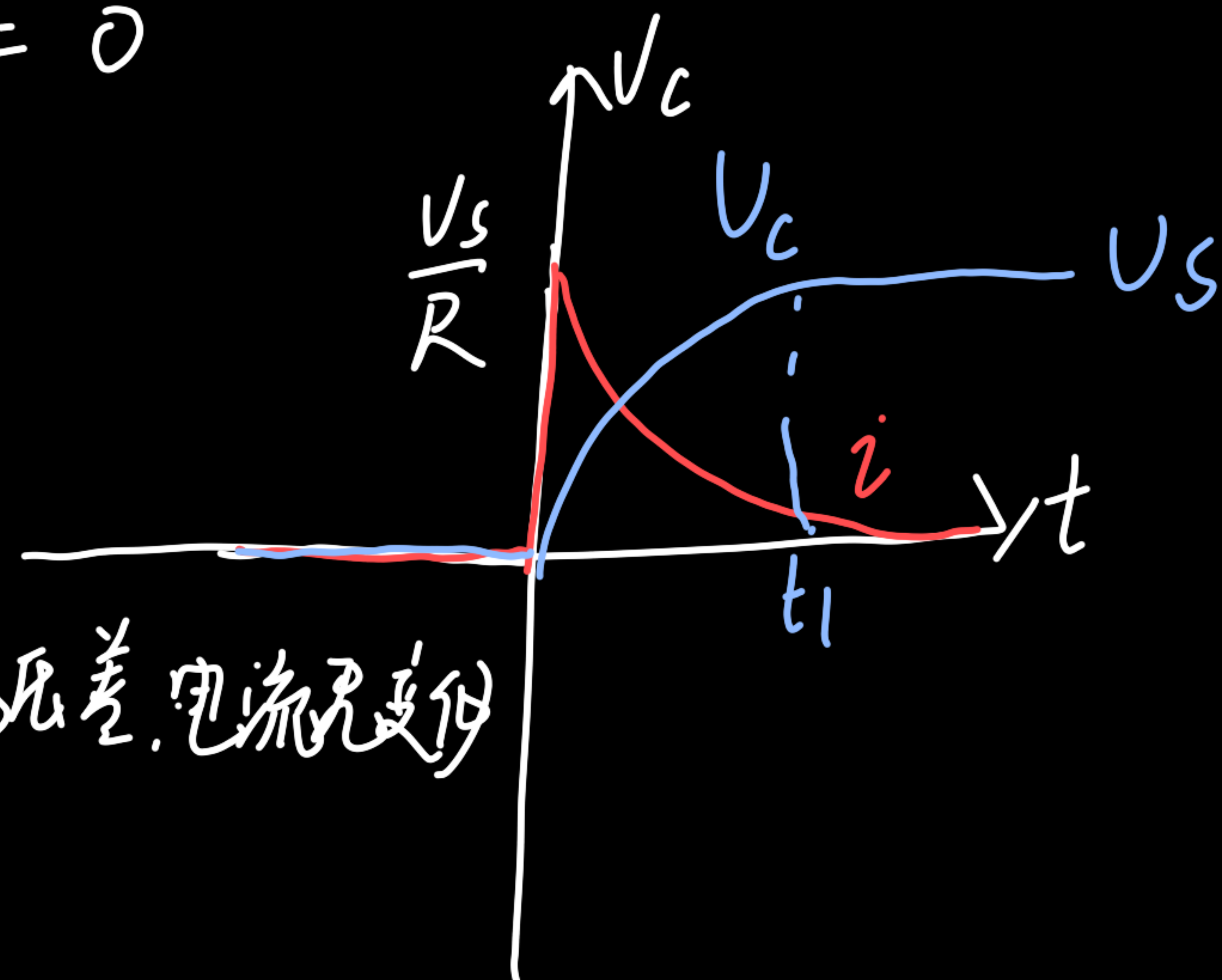$t \rightarrow \infty$ C 相当于开路 (无电压差, 电流无变化)



电感电路

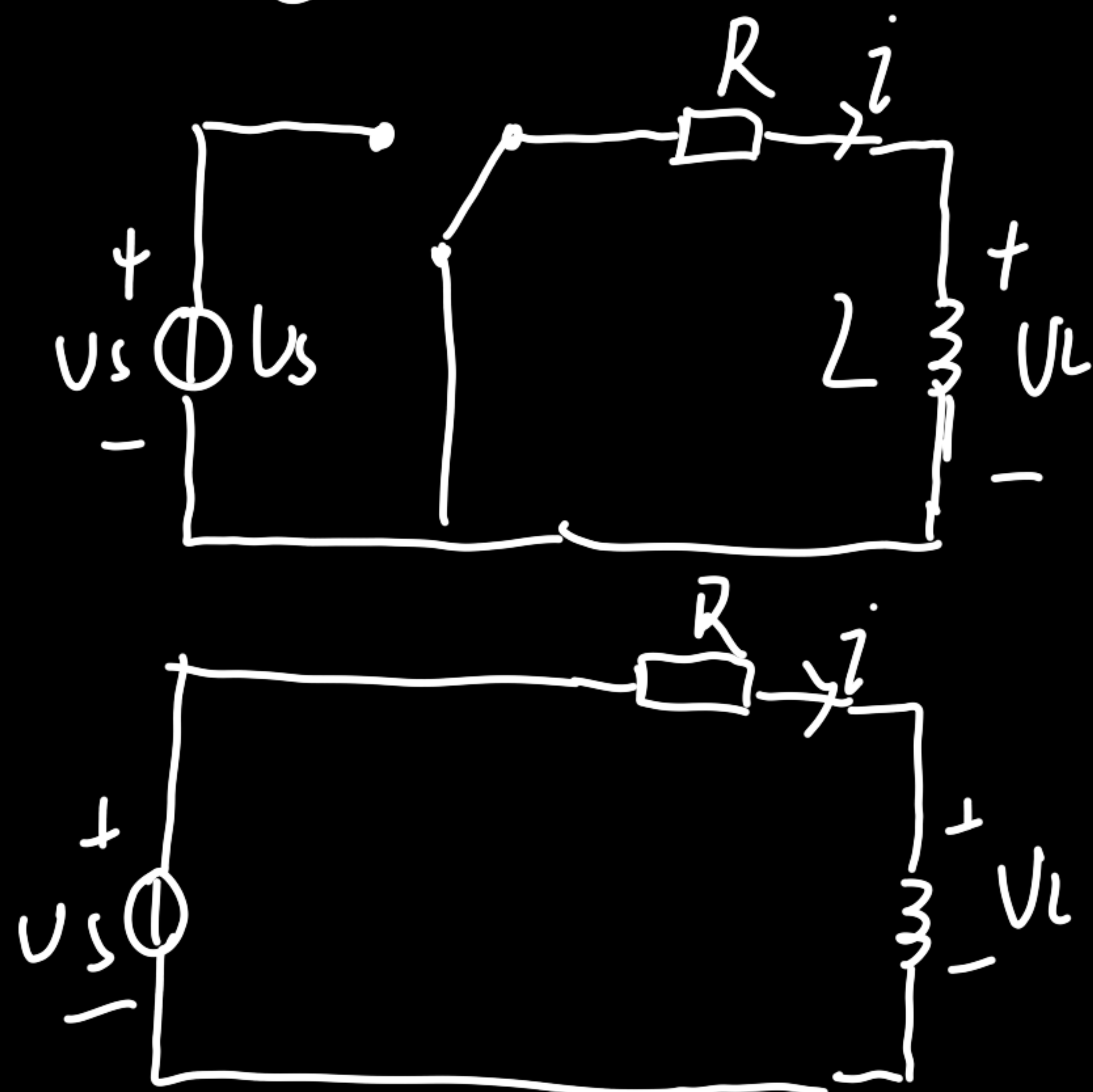

$$i_L(0^-) = i_L(0^+)$$

$$t = 0^- \quad V_L = 0 \quad i = 0$$

$$t = 0^+ \quad i = \frac{U_s}{R}$$

