

电源提供能量

$$\int_0^{\infty} U_s i dt = U_s q = C U_s^2$$

电阻消耗能量

$$\int_0^{\infty} i^2 R dt = \int_0^{\infty} \left( \frac{U_s}{R} e^{-\frac{t}{RC}} \right)^2 R dt$$

$$= \int_0^{\infty} \frac{U_s^2}{R^2} e^{-\frac{2t}{RC}} \cdot R dt = \frac{U_s^2}{R} \int_0^{\infty} e^{-\frac{2t}{RC}} dt$$

$$= \frac{U_s^2}{R} \left[ -\frac{RC}{2} e^{-\frac{2t}{RC}} \right]_0^{\infty} = \frac{U_s^2}{R} \left[ -\frac{RC}{2} \cdot 0 + \frac{RC}{2} \cdot 1 \right]$$

$$= \frac{1}{2} C U_s^2$$

电容储存能量  $\frac{1}{2} C U_s^2$